

Kevin Honeker


3/7

Lab 2

Pre Lab:

Logic equations for a full adder: $Y = A \text{ XOR } B \text{ XOR } C_{in}$

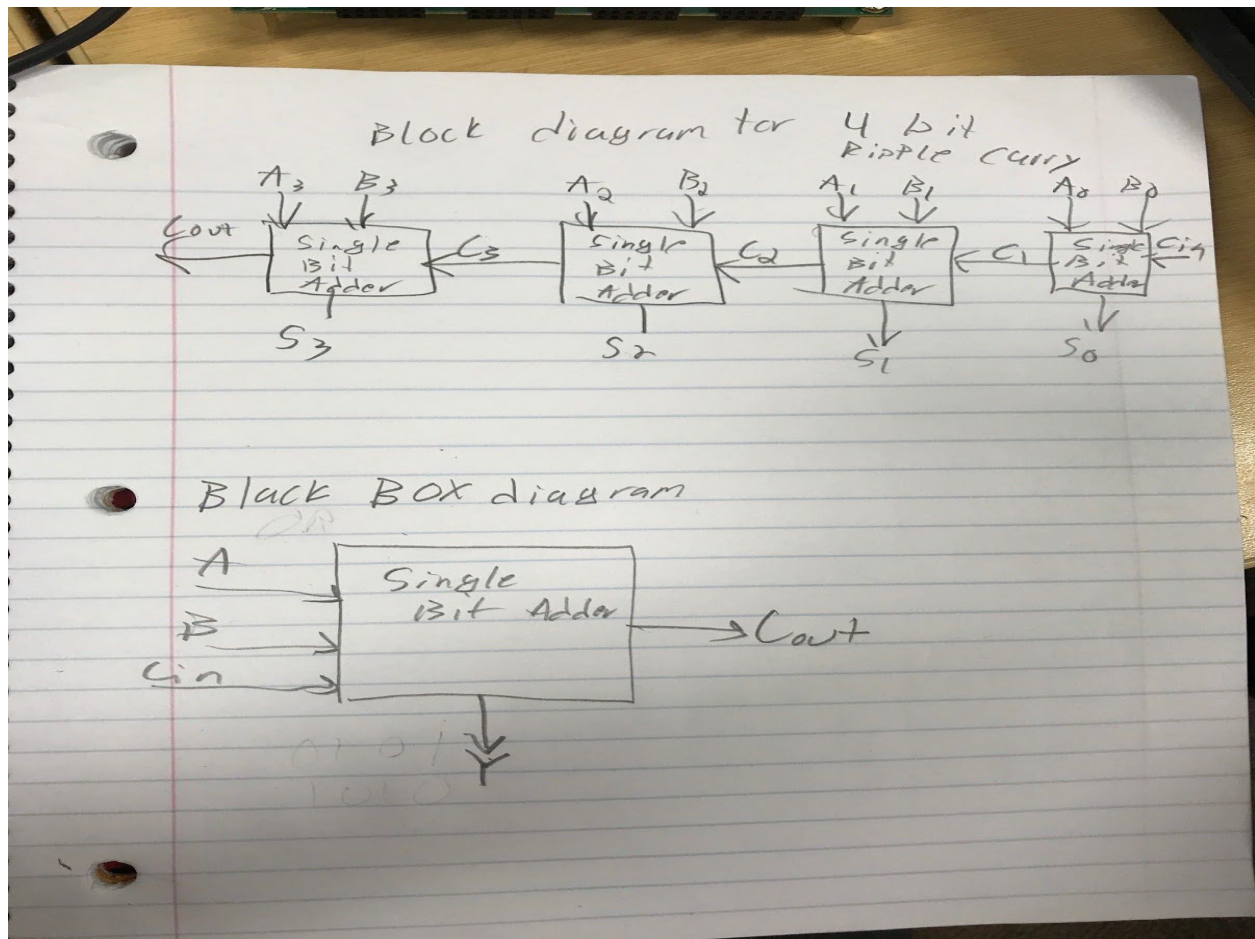$C_{out} = ((A \text{ XOR } B) \text{ AND } C_{in}) \text{ OR } (A \text{ AND } B)$




Purpose: the purpose of this lab is to simulate a 4 bit ripple carry adder and a 16 function ALU.


Part 1

Theory of operation: The circuit should be able to perform 4 bit arithmetic This is the truth table for each single bit adder is:

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

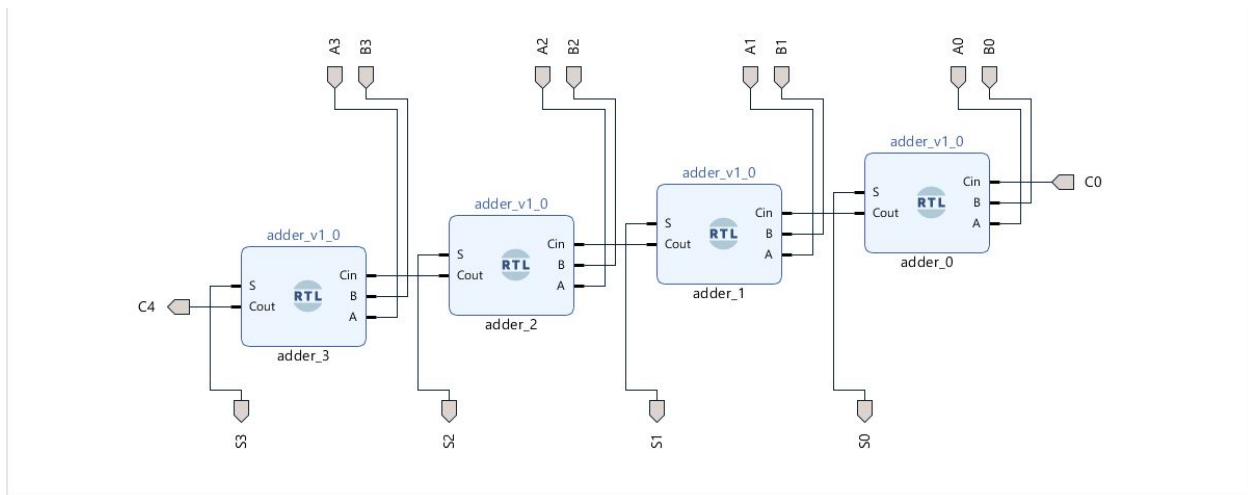Block Diagram that simulated 4 bit ripple carry adder



 

VHDL for Single Bit adder:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
use IEEE.std_logic_unsigned.all;
```

entity adder is

```
    port (A, B, Cin : in std_logic;
          Cout, S   : out std_logic);
```

end adder;

architecture add of adder is

begin

```
S <= (A XOR B) XOR Cin;
Cout <= ((A XOR B) AND Cin) OR (A AND B);
end add;
```

VHDL for 4 bit ripple carry adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
library UNISIM;
use UNISIM.VCOMPONENTS.ALL;
entity ripple_adder is
```

```

port (
  A0 : in STD_LOGIC;
  A1 : in STD_LOGIC;
  A2 : in STD_LOGIC;
  A3 : in STD_LOGIC;
  B0 : in STD_LOGIC;
  B1 : in STD_LOGIC;
  B2 : in STD_LOGIC;
  B3 : in STD_LOGIC;
  C0 : in STD_LOGIC;
  C4 : out STD_LOGIC;
  S0 : out STD_LOGIC;
  S1 : out STD_LOGIC;
  S2 : out STD_LOGIC;
  S3 : out STD_LOGIC
);
attribute CORE_GENERATION_INFO : string;
attribute CORE_GENERATION_INFO of ripple_adder : entity is
"ripple_adder,IP_Integrator,{x_ipVendor=xilinx.com,x_ipLibrary=BlockDiagram,x_ipName=ripple
_adder,x_ipVersion=1.00.a,x_ipLanguage=VHDL,numBlks=4,numReposBlks=4,numNonXlnxBI
ks=0,numHierBlks=0,maxHierDepth=0,numSysgenBlks=0,numHlsBlks=0,numHdlrefBlks=4,num
PkgbdBlks=0,bdsource=USER,synth_mode=OOC_per_IP}";
attribute HW_HANDOFF : string;
attribute HW_HANDOFF of ripple_adder : entity is "ripple_adder.hwdef";
end ripple_adder;

```

architecture STRUCTURE of ripple_adder is

component ripple_adder_adder_0_0 is

```

port (
  A : in STD_LOGIC;
  B : in STD_LOGIC;
  Cin : in STD_LOGIC;
  Cout : out STD_LOGIC;
  S : out STD_LOGIC
);

```

```

end component ripple_adder_adder_0_0;
component ripple_adder_adder_1_0 is

```

```

port (
  A : in STD_LOGIC;
  B : in STD_LOGIC;
  Cin : in STD_LOGIC;
  Cout : out STD_LOGIC;
  S : out STD_LOGIC

```

```

);
end component ripple_adder_adder_1_0;
component ripple_adder_adder_2_0 is
port (
  A : in STD_LOGIC;
  B : in STD_LOGIC;
  Cin : in STD_LOGIC;
  Cout : out STD_LOGIC;
  S : out STD_LOGIC
);
end component ripple_adder_adder_2_0;
component ripple_adder_adder_3_0 is
port (
  A : in STD_LOGIC;
  B : in STD_LOGIC;
  Cin : in STD_LOGIC;
  Cout : out STD_LOGIC;
  S : out STD_LOGIC
);
end component ripple_adder_adder_3_0;
signal A0_1 : STD_LOGIC;
signal A1_1 : STD_LOGIC;
signal A2_1 : STD_LOGIC;
signal A3_1 : STD_LOGIC;
signal B0_1 : STD_LOGIC;
signal B1_1 : STD_LOGIC;
signal B2_1 : STD_LOGIC;
signal B3_1 : STD_LOGIC;
signal C0_1 : STD_LOGIC;
signal adder_0_Cout : STD_LOGIC;
signal adder_0_S : STD_LOGIC;
signal adder_1_Cout : STD_LOGIC;
signal adder_1_S : STD_LOGIC;
signal adder_2_Cout : STD_LOGIC;
signal adder_2_S : STD_LOGIC;
signal adder_3_Cout : STD_LOGIC;
signal adder_3_S : STD_LOGIC;
begin
  A0_1 <= A0;
  A1_1 <= A1;
  A2_1 <= A2;
  A3_1 <= A3;
  B0_1 <= B0;

```

```

B1_1 <= B1;
B2_1 <= B2;
B3_1 <= B3;
C0_1 <= C0;
C4 <= adder_3_Cout;
S0 <= adder_0_S;
S1 <= adder_1_S;
S2 <= adder_2_S;
S3 <= adder_3_S;
adder_0: component ripple_adder_adder_0_0
    port map (
        A => A0_1,
        B => B0_1,
        Cin => C0_1,
        Cout => adder_0_Cout,
        S => adder_0_S
    );
adder_1: component ripple_adder_adder_1_0
    port map (
        A => A1_1,
        B => B1_1,
        Cin => adder_0_Cout,
        Cout => adder_1_Cout,
        S => adder_1_S
    );
adder_2: component ripple_adder_adder_2_0
    port map (
        A => A2_1,
        B => B2_1,
        Cin => adder_1_Cout,
        Cout => adder_2_Cout,
        S => adder_2_S
    );
adder_3: component ripple_adder_adder_3_0
    port map (
        A => A3_1,
        B => B3_1,
        Cin => adder_2_Cout,
        Cout => adder_3_Cout,
        S => adder_3_S
    );
end STRUCTURE;

```

Test Bench

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity test_ripple_adder is

end test_ripple_adder;

architecture TB of test_ripple_adder is

component ripple_adder is

port (

A0 : in STD_LOGIC;

A1 : in STD_LOGIC;

A2 : in STD_LOGIC;

A3 : in STD_LOGIC;

B0 : in STD_LOGIC;

B1 : in STD_LOGIC;

B2 : in STD_LOGIC;

B3 : in STD_LOGIC;

C0 : in STD_LOGIC;

C4 : out STD_LOGIC;

S0 : out STD_LOGIC;

S1 : out STD_LOGIC;

S2 : out STD_LOGIC;

S3 : out STD_LOGIC

);

end component ripple_adder;

signal A0 : STD_LOGIC;

signal A1 : STD_LOGIC;

signal A2 : STD_LOGIC;

signal A3 : STD_LOGIC;

signal B0 : STD_LOGIC;

signal B1 : STD_LOGIC;

signal B2 : STD_LOGIC;

signal B3 : STD_LOGIC;

signal C0 : STD_LOGIC;

signal C4 : STD_LOGIC;

signal S0 : STD_LOGIC;

signal S1 : STD_LOGIC;

signal S2 : STD_LOGIC;

signal S3 : STD_LOGIC;

```
begin
```

```
test : process
```

```
begin
```

```
--wait for 10 ns;
```

```
  A0<='0';
```

```
  A1<='0';
```

```
  A2<='0';
```

```
  A3<='0';
```

```
  B0<='0';
```

```
  B1<='0';
```

```
  B2<='0';
```

```
  B3<='0';
```

```
  C0<='0';
```

```
  wait for 10 ns;
```

```
  A0<='1';    --A = 0001
```

```
  B0<='1';    --B = 0001
```

```
  wait for 10 ns;
```

```
  A2<='1';    --A = 0101
```

```
  B3<='1';    --B = 1101
```

```
  B2<='1';
```

```
  C0<='1';
```

```
  wait for 10 ns;
```

```
  A0<='0';
```

```
  B0<='0';    --B = 1100
```

```
  A3<='1';    --A = 1100
```

```
  wait for 10 ns;
```

```
  A3<='0';
```

```
  A2<='0';
```

```
  A1<='1';
```

```
  A0<='1';    -- A = 0011
```

```
  C0<='0';
```

```
  Wait for 10 ns;
```

```
  C0<='1';
```

```
end process;
```

```
DUT: component ripple_adder port map (
```

```
  A0 => A0,
```

```
  A1 => A1,
```

```
  A2 => A2,
```



```

A3 => A3,
B0 => B0,
B1 => B1,
B2 => B2,
B3 => B3,
C0 => C0,
C4 => C4,
S0 => S0,
S1 => S1,
S2 => S2,
S3 => S3
);

```

```


end TB;

```


Part 2

Theory of Operation: The circuit should be have as the 16 function 4 bit ALU whose functions are specified in the lab instructions.


Elaboration Schematic:

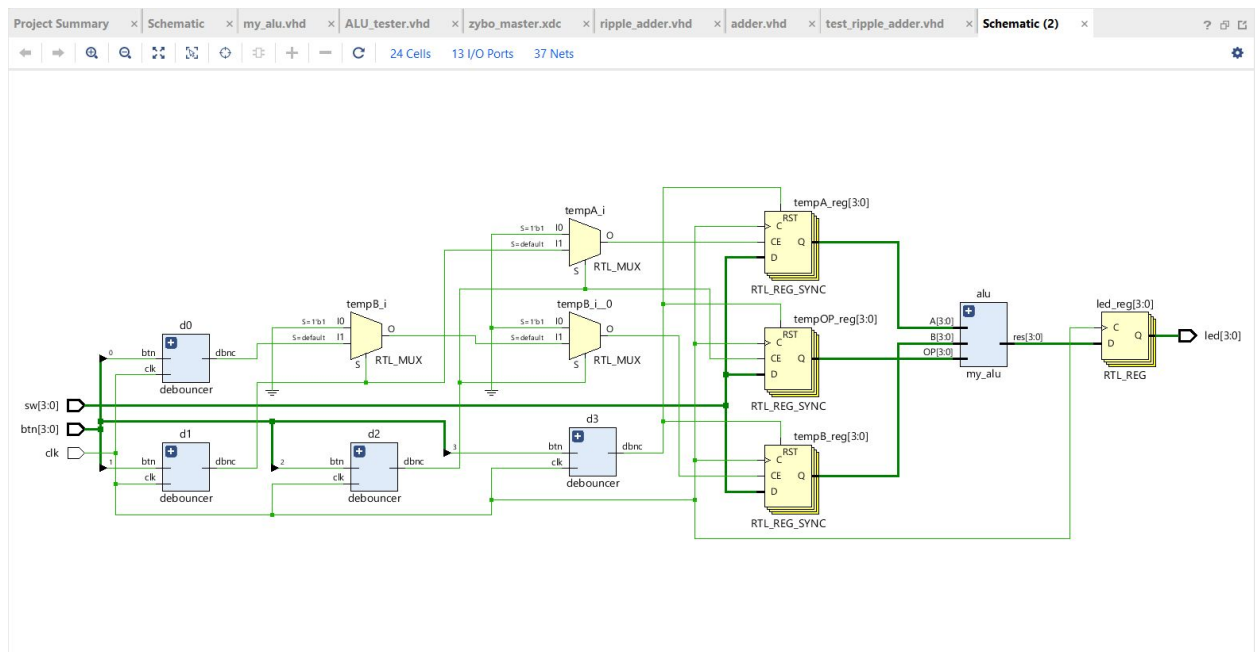

Synthesis Schematic

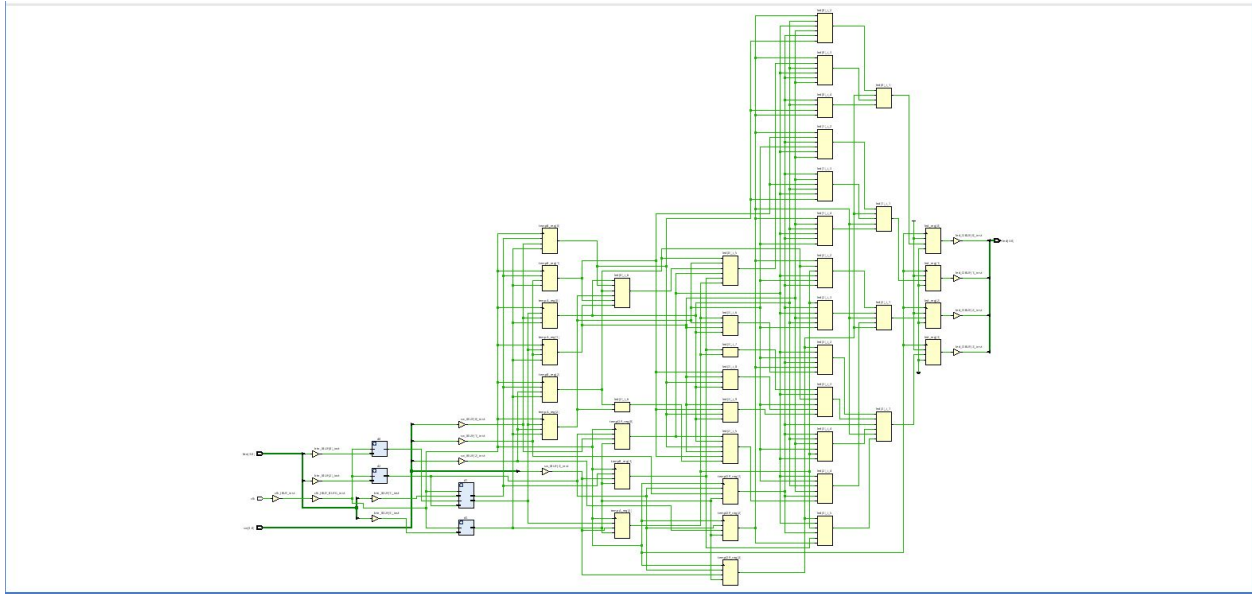

Power Graphs and utilization table

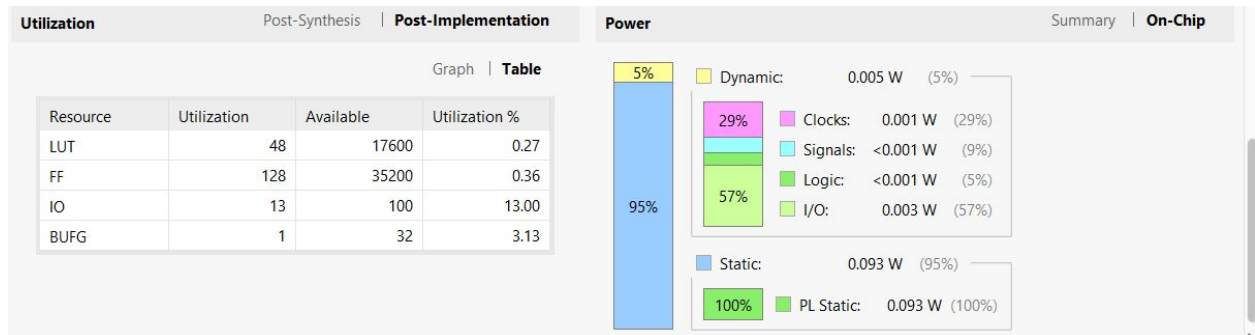

VHDL Code for my_ALU

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.std_logic_unsigned.all;
use IEEE.NUMERIC_STD.ALL;

entity my_alu is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          OP : in STD_LOGIC_VECTOR (3 downto 0);
```

```
        res : out STD_LOGIC_VECTOR (3 downto 0));  
end my_alu;
```

architecture Behavioral of my_alu is

```
begin  
process (OP)  
begin  
    case OP is  
        when "0000" => res <= A+B;  
        when "0001" => res <= A-B;  
        when "0010" => res <= A+1;  
        when "0011" => res <= A-1;  
        when "0100" => res <= 0-A;  
        when "0101" =>  
            if unsigned(A)>unsigned(B) then  
                res <= "0001";  
            else  
                res <= "0000";  
            end if;  
  
        when "0110" => res<= A(2 downto 0)&'0';  
        when "0111" => res<= '0'&A(3 downto 1);  
        when "1000" => res<= '1'&A(3 downto 1);  
        when "1001" => res<= not A;  
        when "1010" => res<= A AND B;  
        when "1011" => res<= A OR B;  
        when "1100" => res<= A XOR B;  
        when "1101" => res<= A XNOR B;  
        when "1110" => res<= A NAND B;  
        when "1111" => res<= A NOR B;  
        when others => res<= "0000";  
  
    end case;  
  
end process;  
end Behavioral;
```

VHDL Code for ALU_tester

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
entity ALU_tester is
```

```
    Port (btn, sw : in std_logic_vector(3 downto 0);
```

```
          led    : out std_logic_vector(3 downto 0);
```

```
          clk    : in std_logic);
```

```
end ALU_tester;
```

```
architecture alu_test of ALU_tester is
```

```
    signal dbnc0, dbnc1, dbnc2, dbnc3 : std_logic;
```

```
    signal result, tempA, tempB, tempOP : std_logic_vector(3 downto 0);
```

```
    component debouncer
```

```
        port ( btn, clk : in std_logic;
```

```
              dbnc    : out std_logic);
```

```
    end component;
```

```
    component my_alu
```

```
        port( A : in STD_LOGIC_VECTOR (3 downto 0);
```

```
              B : in STD_LOGIC_VECTOR (3 downto 0);
```

```
              OP : in STD_LOGIC_VECTOR (3 downto 0);
```

```
              res : out STD_LOGIC_VECTOR (3 downto 0));
```

```
    end component;
```

```
begin
```

```
    d0 : debouncer
```

```
        port map( btn => btn(0),
```

```
                  clk => clk,
```

```
                  dbnc => dbnc0);
```

```
    d1 : debouncer
```

```
        port map (btn => btn(1),
```

```
                  clk => clk,
```

```
                  dbnc => dbnc1);
```

```
    d2 : debouncer
```

```
        port map ( btn => btn(2),
```

```
                  clk=> clk,
```

```
                  dbnc => dbnc2);
```

```
    d3 : debouncer
```

```
        port map (btn => btn(3),
```

```

        clk => clk,
        dbnc => dbnc3);

alu : my_alu
port map ( A => tempA,
          B => tempB,
          OP => tempOP,
          res => result);

process (clk)
begin
    if clk='1' and clk'event then
        if dbnc3 ='1' then
            tempA<="0000";
            tempB<="0000";
            tempOP<="0000";
        elsif dbnc2 = '1' then
            tempOP<=sw;
        elsif dbnc1 = '1' then
            tempA<=sw;
        elsif dbnc0 = '1' then
            tempB<=sw;
        end if;
        led<=result;
    end if;
end process;

end alu_test;

```

Zybo master XDC file

#Clock signal

```

set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports { clk }];
#IO_L11P_T1_SRCC_35 Sch=sysclk
create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports { clk }];

```

##Switches

```

set_property -dict { PACKAGE_PIN G15  IOSTANDARD LVCMOS33 } [get_ports { sw[0] }];
#IO_L19N_T3_VREF_35 Sch=SW0
set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports { sw[1] }];
#IO_L24P_T3_34 Sch=SW1
set_property -dict { PACKAGE_PIN W13  IOSTANDARD LVCMOS33 } [get_ports { sw[2] }];
#IO_L4N_T0_34 Sch=SW2

```

```
set_property -dict { PACKAGE_PIN T16  IOSTANDARD LVCMOS33 } [get_ports { sw[3] }];  
#IO_L9P_T1_DQS_34 Sch=SW3
```

##Buttons

```
set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports { btn[0] }];  
#IO_L20N_T3_34 Sch=BTN0  
set_property -dict { PACKAGE_PIN P16  IOSTANDARD LVCMOS33 } [get_ports { btn[1] }];  
#IO_L24N_T3_34 Sch=BTN1  
set_property -dict { PACKAGE_PIN V16  IOSTANDARD LVCMOS33 } [get_ports { btn[2] }];  
#IO_L18P_T2_34 Sch=BTN2  
set_property -dict { PACKAGE_PIN Y16  IOSTANDARD LVCMOS33 } [get_ports { btn[3] }];  
#IO_L7P_T1_34 Sch=BTN3
```

##LEDs

```
set_property -dict { PACKAGE_PIN M14  IOSTANDARD LVCMOS33 } [get_ports { led[0] }];  
#IO_L23P_T3_35 Sch=LED0  
set_property -dict { PACKAGE_PIN M15  IOSTANDARD LVCMOS33 } [get_ports { led[1] }];  
#IO_L23N_T3_35 Sch=LED1  
set_property -dict { PACKAGE_PIN G14  IOSTANDARD LVCMOS33 } [get_ports { led[2] }];  
#IO_0_35=Sch=LED2  
set_property -dict { PACKAGE_PIN D18  IOSTANDARD LVCMOS33 } [get_ports { led[3] }];  
#IO_L3N_T0_DQS_AD1N_35 Sch=LED3
```

The segment of code is the uncomment parts of the xdc file that allowed my designs to work on the Zybo board.

Discussion:

In this lab I learned about the functions and operations that are defined in the numeric_std library. I also learned that Vivado can generate test bench files and design sources from block diagrams